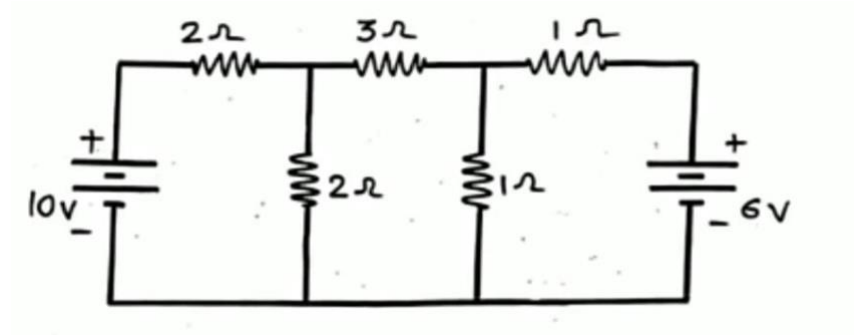



SECTION C

CIRCUITS FOR BEE


Find the current and power consumed by 3 ohm resistor for the circuit given below:



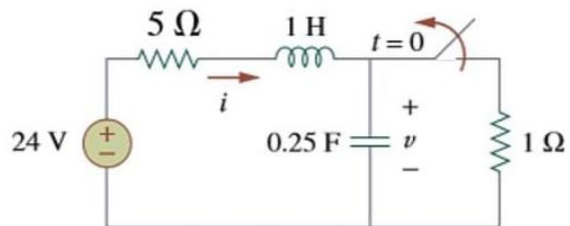For the circuit given below find $v(t)$ and $i(t)$ for $t > 0$:



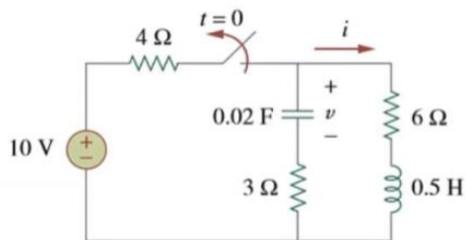
Find $i(t)$ in the circuit assuming that the circuit has reached a steady state at $t = 0^-$.



Find the current flowing through the load resistance when it is equal to 16 ohm using Thevenin Theorem:



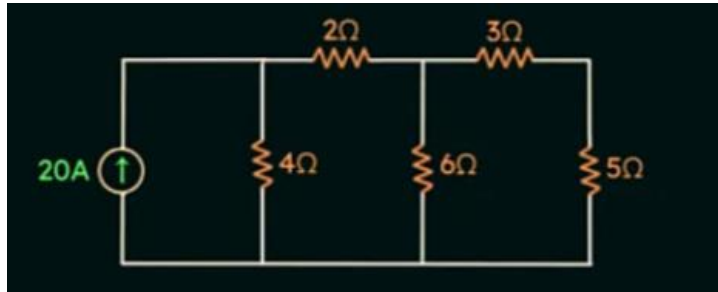Find the current flowing through 5 ohm resistor using Norton Theorem:



The circuit contains a switch that can be used to connect and disconnect a battery. The switch has been open for a very long time. At $t=0$ the switch closes, and then at $t=50\text{ms}$ it opens again. Determine capacitor voltage as a function of time.

$R_1=R_2=1000\text{ ohm}$

$R_3=500\text{ ohm}$

$C= 25\text{ microfarad}$

